

习题课

1、高频小信号放大器电路如下图所示。已知工作频率

$$f_0 = 30\text{MHz}, L_{13} = 1\mu\text{H}$$


；C与 L_{13} 组成的谐振回路空载品质因子 $Q_0 = 100$ ； $N_{13} = 50$ 匝， $N_{23} = 25$ 匝； $N_{45} = 10$ 匝； $R = 10\text{k}\Omega$ ， $R_L = 1\text{k}\Omega$ 。三极管的y参数为：


$$y_{ie} = (1.6 + j4.0)\text{ms}, y_{fe} = (36.4 - j42.4)\text{ms}, y_{oe} = (0.072 + j0.6)\text{ms}$$

忽略 y_{re}


(1) 画出交流等效电路
(要求在图中对应标出1和3节点)；

(2) 计算谐振电压增益
 A_{v_0} 、有载品质因子 Q_L 、
通频带。

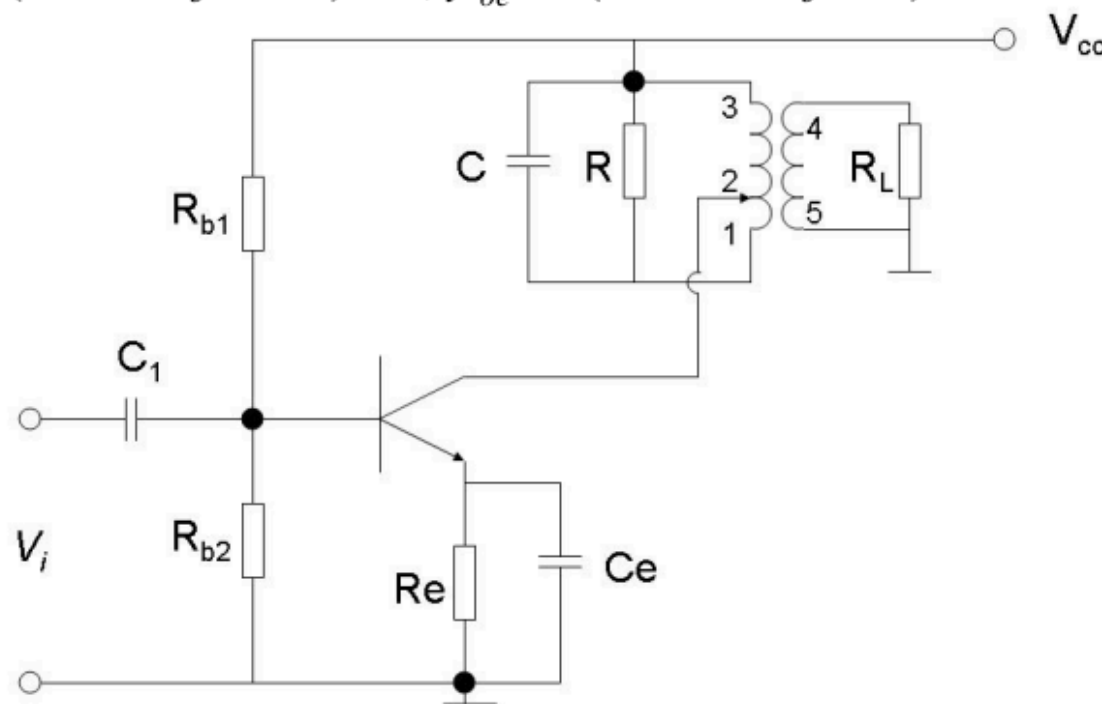

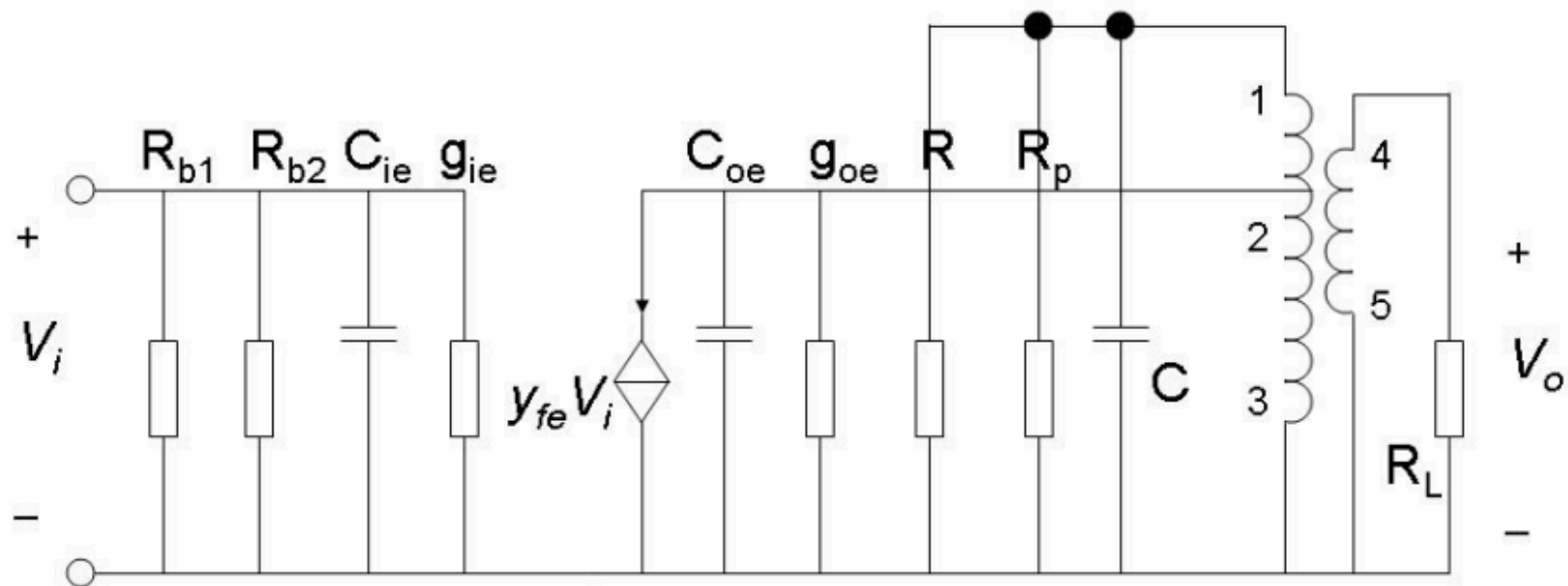

(a)

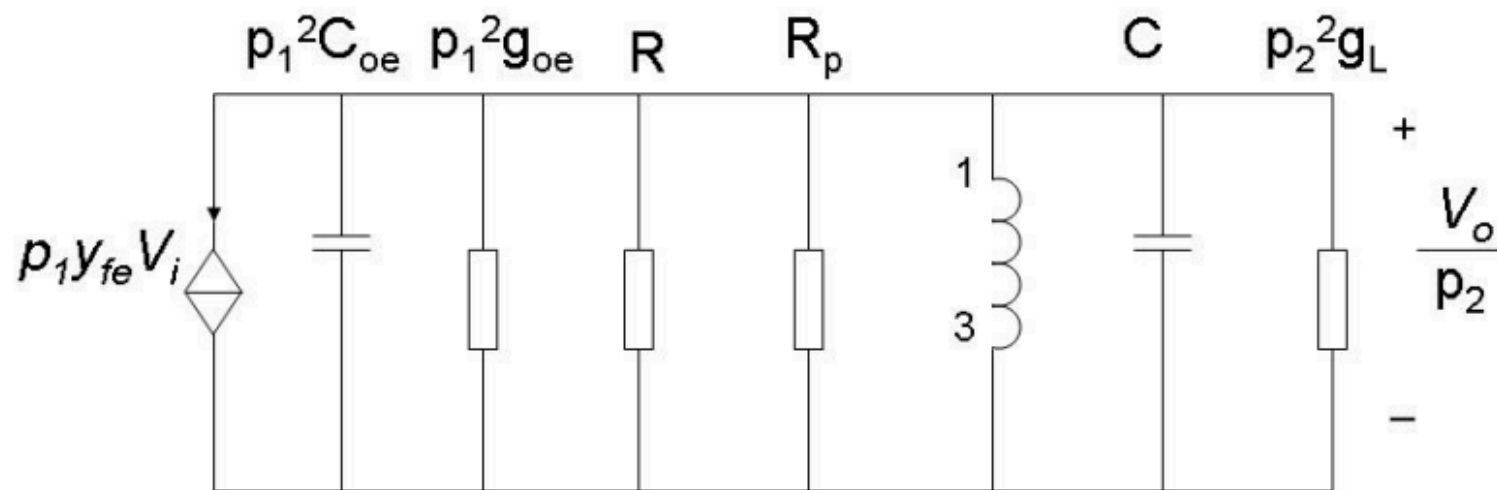

(b)

$$(2) \quad p_1 = \frac{N_{23}}{N_{13}} = \frac{25}{50} = 0.5 \quad p_2 = \frac{N_{45}}{N_{13}} = \frac{10}{50} = 0.2$$

$$G_p = \frac{1}{\omega_0 L_{13} Q_0} = \frac{1}{2\pi \times 30 \times 10^6 \times 1 \times 10^{-6} \times 100} = 53(\mu S)$$

$$\therefore g_{\Sigma} = G_p + p_1^2 g_{oe} + p_2^2 \frac{1}{R_L} = 63 \times 10^{-6} + 0.5^2 \times 0.072 \times 10^{-3} + 0.2^2 \times \frac{1}{620} = 145(\mu S)$$

$$\therefore |A_{v0}| = \frac{p_1 p_2 |y_{fe}|}{g_{\Sigma}} = \frac{0.5 \times 0.2 \times 50 \times 10^{-3}}{145 \times 10^{-6}} = 34.5$$

$$\therefore Q_L = \frac{1}{\omega_0 L_{13} g_{\Sigma}} = \frac{1}{2\pi \times 30 \times 10^6 \times 1 \times 10^{-6} \times 145 \times 10^{-6}} = 36.6$$


$$\therefore 2\Delta f_{0.7} = \frac{f_0}{Q_L} = \frac{30 \times 10^6}{36.6} = 820(KHz)$$

2、如下图所示，已知 $v_s = V_{sm} \cos \omega_s t$

$$v_0 = V_{0m} \cos \omega_0 t$$

$$V_{0m} \gg V_{sm}$$

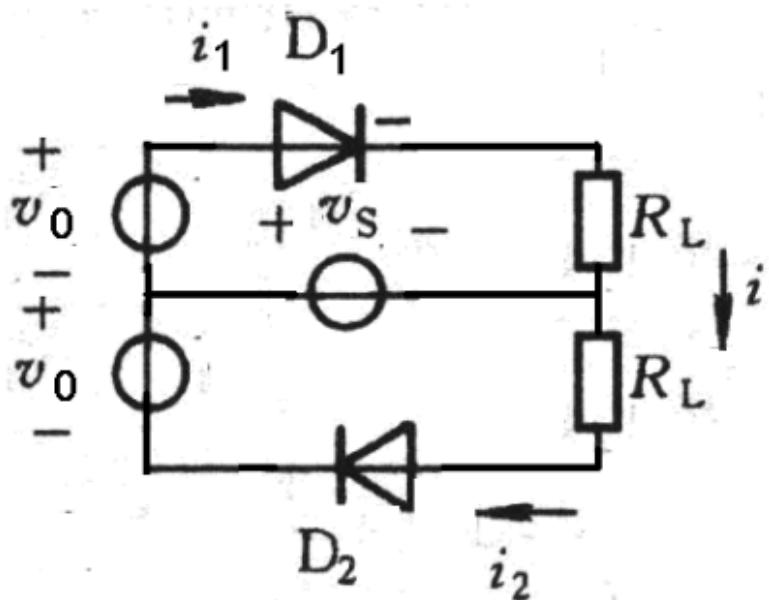二极管工作在受 v_0 控制的开关状态，二极管 **D1, D2** 的伏安特性相同，均为从原点出发，斜率为 g_D 的直线。推导输出电流 i 的表达式，并分析其中的频谱成分。



解: $r_d = \frac{1}{g_D}$


$$i_1 = \frac{1}{r_d + R_L} s(t)(v_s + v_0) \quad (2 \text{ 分})$$


$$i_2 = \frac{1}{r_d + R_L} s(t)(v_0 - v_s) \quad (2 \text{ 分})$$

$$i = i_1 + i_2 = 2 \frac{1}{r_d + R_L} s(t)v_0 \quad (2 \text{ 分})$$

$$i = 2 \frac{1}{r_d + R_L} \left(\frac{1}{2} + \frac{2}{\pi} \cos \omega_0 t - \frac{2}{3\pi} \cos 3\omega_0 t + \dots \right) V_{0m} \cos \omega_0 t \quad (2 \text{ 分})$$

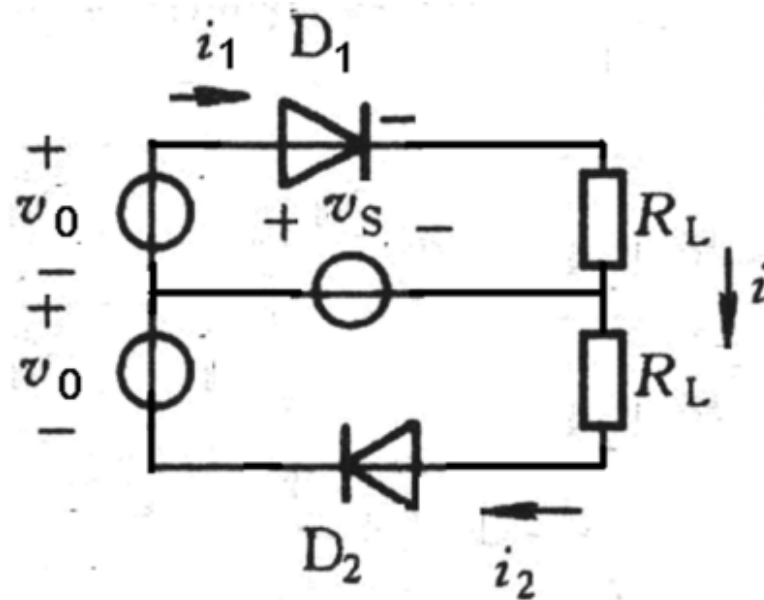输出电流的频谱成分为 $\omega_0, 2n\omega_0 (n=1,2,3,\dots)$ (2 分)




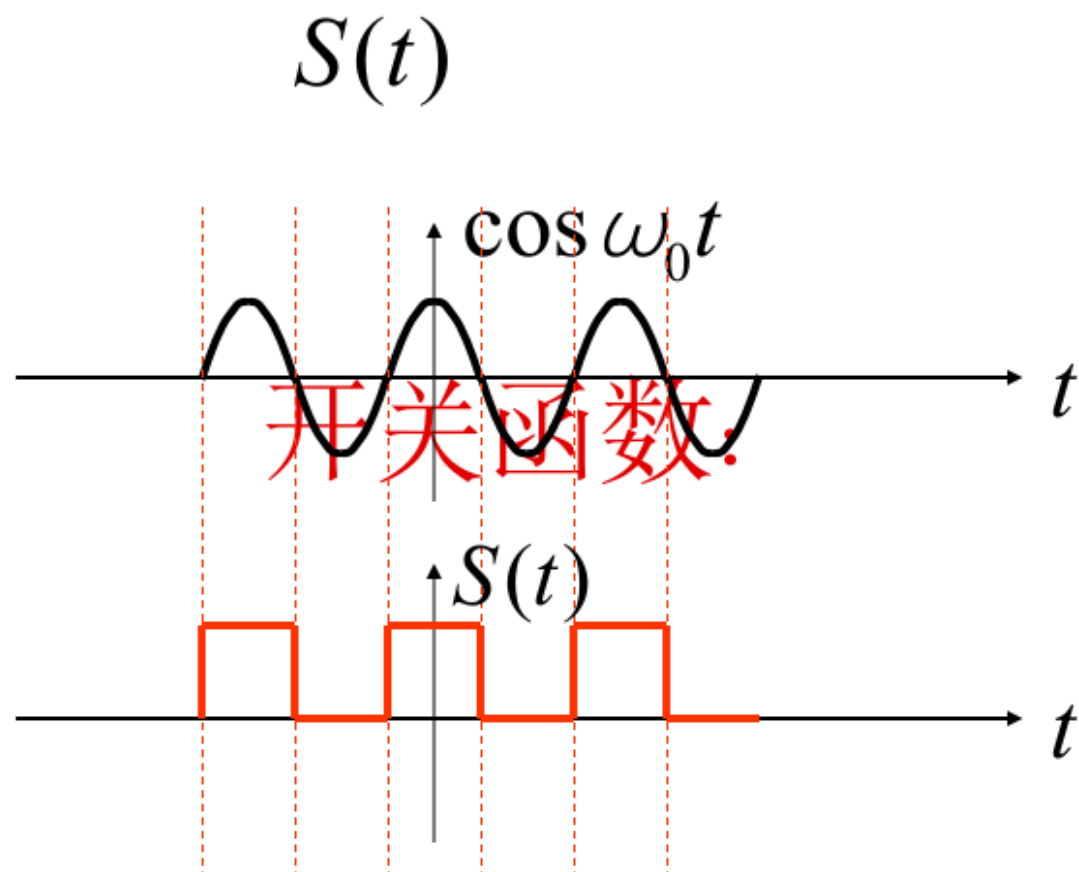

$\because S(t)$ 为一周期函数,所以可以用付立叶级数展开


$$S(t) = \frac{1}{2} + \frac{2}{\pi} \cos \omega_0 t - \frac{2}{3\pi} \cos 3\omega_0 t + \frac{2}{5\pi} \cos 5\omega_0 t \cdots$$
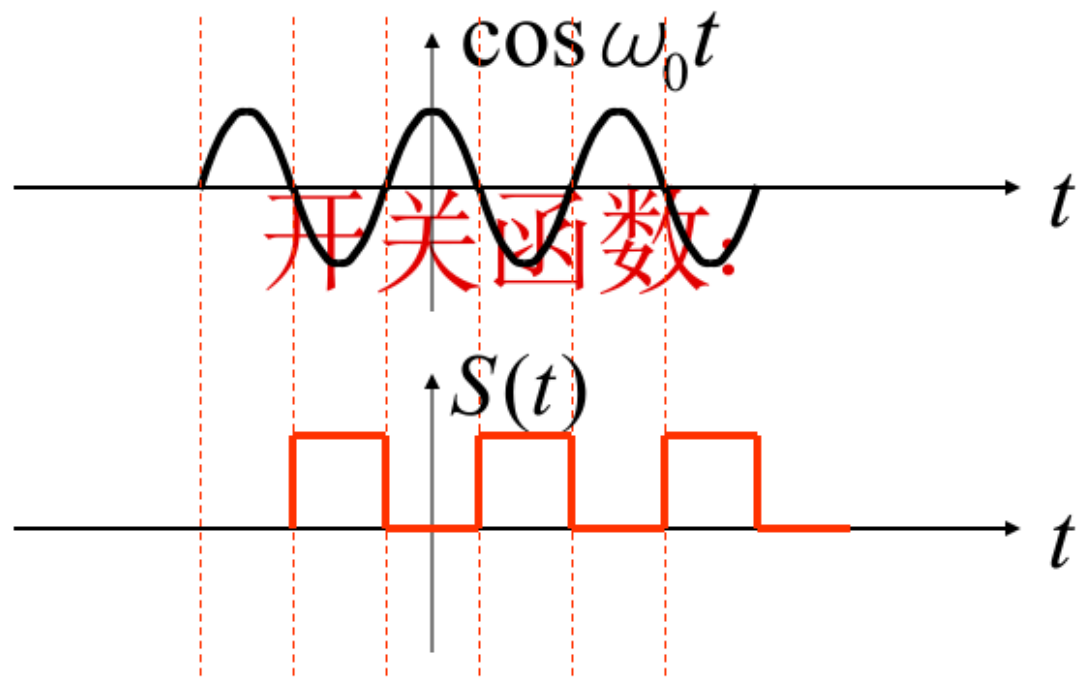
$$S^*(t) = S(t - \frac{T}{2}) = S(t + \frac{T}{2})$$



$$S^*(t) = \frac{1}{2} - \frac{2}{\pi} \cos \omega_0 t + \frac{2}{3\pi} \cos 3\omega_0 t - \frac{2}{5\pi} \cos 5\omega_0 t \cdots$$

$$S'(t) = S(t) - S^*(t)$$

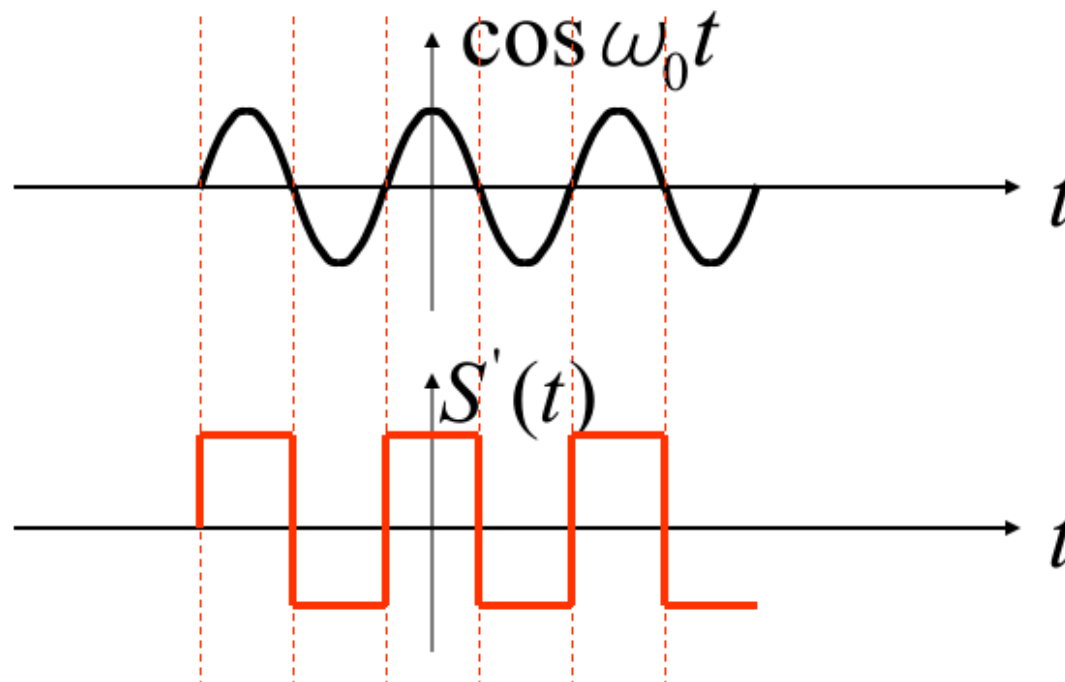


$$S'(t) = \frac{4}{\pi} \cos \omega_0 t - \frac{4}{3\pi} \cos 3\omega_0 t + \frac{4}{5\pi} \cos 5\omega_0 t \cdots$$

某谐振功放的动态特性曲线如图所示，并且已知 $\theta_c = 90^\circ$,

$$a_0(90^\circ) = 0.32 \quad a_1(90^\circ) = 0.5$$

(1) 问该放大器工作在什么状态？求此时的 P_o 、 P_{dc} 、效率、 R_p

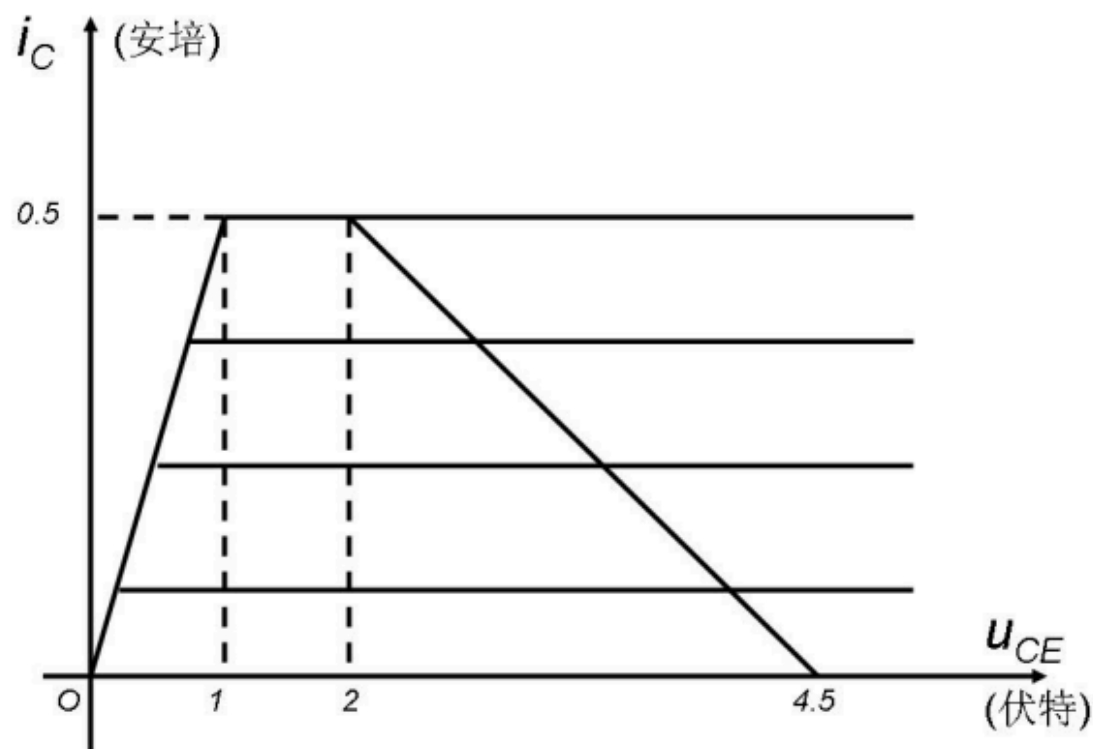2) 若要输出功率达到最大，问放大器应工作在什么状态？ R_p 应如何调整？调整到多大？
(调整 R_p 的时候 θ_c 不变)



(1) 放大器工作在欠压状态, 从图上可读出:

$$i_{C\max} = 0.5A \quad V_{CC} = 4.5(V) \quad V_{cm} = 4.5 - 2 = 2.5(V)$$

$$I_{cm1} = i_{C\max} a_1(\theta) = 0.5 \times 0.5 = 0.25(A)$$

$$I_{cm0} = i_{C\max} a_0(\theta) = 0.5 \times 0.32 = 0.16(A)$$

$$P_O = \frac{1}{2} I_{cm1} V_{cm} = \frac{1}{2} \times 0.25 \times 2.5 = 0.3125(W)$$

$$P_{\Sigma} = I_{cm0} V_{CC} = 0.16 \times 4.5 = 0.72(W)$$

$$P_C = P_{\Sigma} - P_O = 0.72 - 0.3125 = 0.4075(W)$$

$$\eta_C = \frac{P_O}{P_{\Sigma}} = 43\% \quad R_p = \frac{V_{cm}}{I_{cm1}} = 10\Omega$$

(2) 若要输出功率最大，应该工作在临界状态。 R_p 应该增大才能从欠压变到临界。从图上看，应该使 V_{cm} 调到3.5V（此时负载线的左端恰好与拐点相交）。此时

$$R_p = \frac{V'_{cm}}{I_{cm1}} = 14\Omega$$

4、有一调幅波表达式为：

$$u(t)=2 \left(1+0.2\cos 2\pi \times 1000 t +0.4\cos 4\pi \times 1000 t \right) \cos 2\pi \times 10^6 t \text{伏}$$

。要求：

- (1) 画出调幅信号的频谱图，标出各频率分量及幅度；
- (2) 求频带宽度；
- (3) 当负载电阻为1欧姆时，求载波功率、各边带功率之和、以及总功率。

- (1) $\omega_0 = 2\pi \times 10^6$ $V_0 = 2$

$$\Omega_1 = 2\pi \times 1000 \quad ma_1 = 0.2$$

$$\Omega_2 = 4\pi \times 1000 \quad ma_2 = 0.4$$

$$\frac{1}{2}ma_1V_0 = \frac{1}{2} \times 0.2 \times 2 = 0.2$$

$$\frac{1}{2}ma_2V_0 = \frac{1}{2} \times 0.4 \times 2 = 0.4$$

频率分量及幅度为:


$$\omega_0 - \Omega_2 = 2\pi \times (10^6 - 2000) \quad 0.4$$

$$\omega_0 - \Omega_1 = 2\pi \times (10^6 - 1000) \quad 0.2$$

$$\omega_0 = 2\pi \times 10^6 \quad 2$$

$$\omega_0 + \Omega_1 = 2\pi \times (10^6 + 1000) \quad 0.2$$
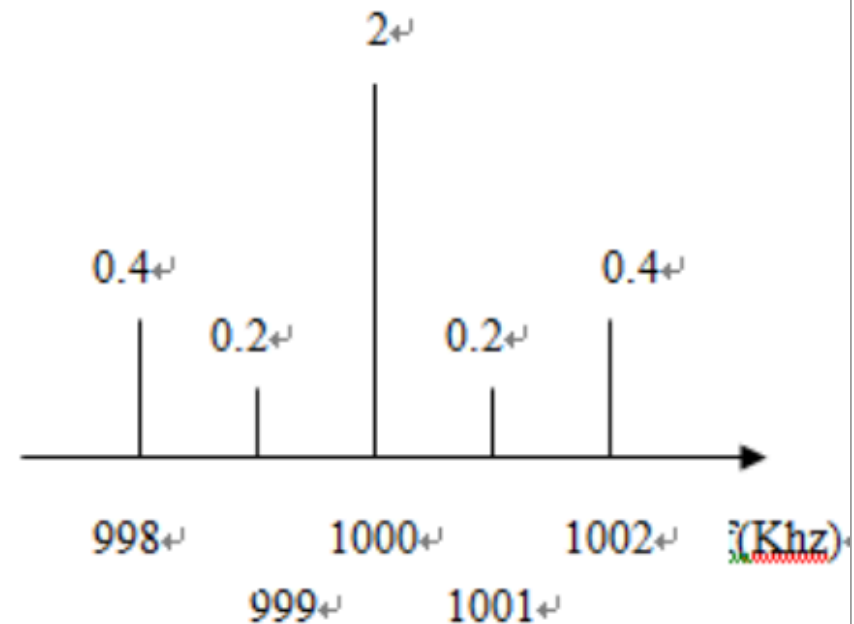
$$\omega_0 + \Omega_2 = 2\pi \times (10^6 + 2000) \quad 0.4$$



$$BW = 2\Omega_2 = 8\pi \times 1000$$

$$P_{OT} = \frac{V_0^2}{2R} = \frac{2^2}{2 \times 1} = 2(W)$$

$$P_{(\omega \pm \Omega)} = \frac{1}{2} m_{a1}^2 P_{OT} + \frac{1}{2} m_{a2}^2 P_{OT} = \frac{1}{2} \times 0.2^2 \times 2 + \frac{1}{2} \times 0.4^2 \times 2 = 0.2(W)$$

$$Po = P_{OT} + P_{(\omega \pm \Omega)} = 2 + 0.2 = 2.2(W)$$